

# **Introduction to Embedded System Design**

## **MSP430 Switch Interfacing**

Dhananjay V. Gadre

Associate Professor

ECE Division

Netaji Subhas University of  
Technology, New Delhi

Badri Subudhi

Assistant Professor

Electrical Engineering Department



Indian Institute of Technology,  
Jammu

# Digital Switch Interfacing

Possible ways for a switch connection :

- Pull up configuration
- Pull down configuration

# Digital Switch Interfacing

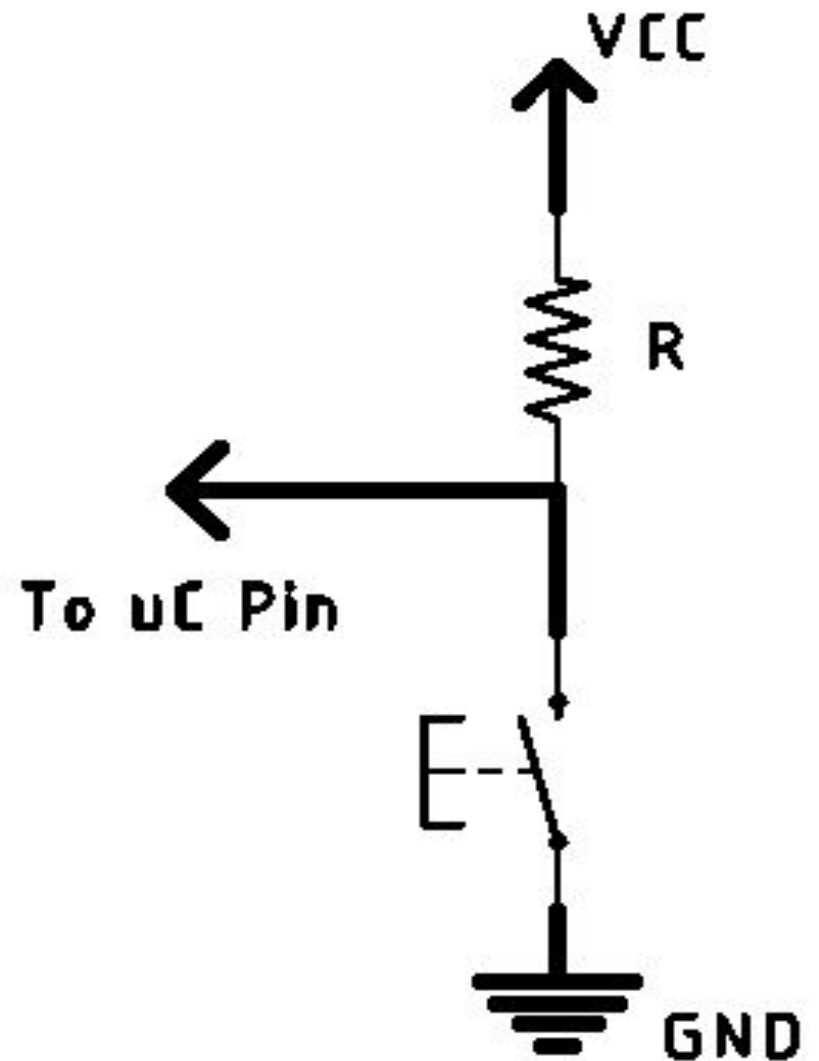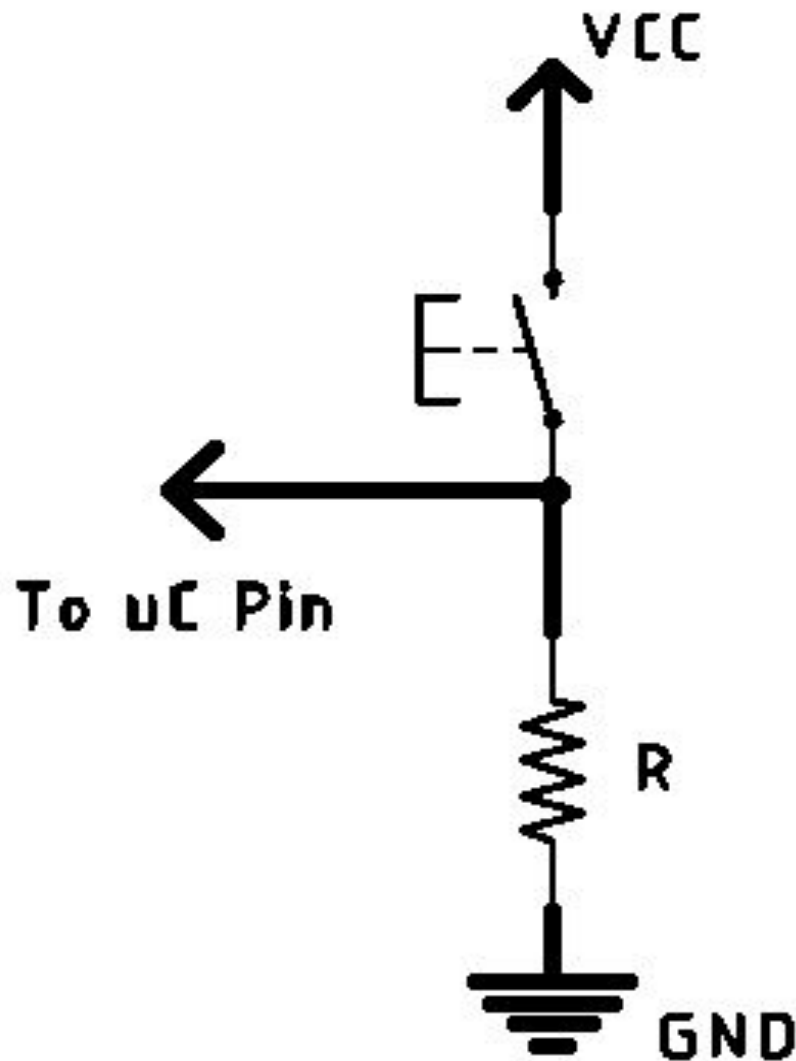

# Digital Input Registers

The MSP430 registers required for switch inputs:

- P<sub>x</sub>DIR
- P<sub>x</sub>IN
- P<sub>x</sub>OUT
- P<sub>x</sub>REN

# Reading inputs


Suppose there is a switch connected to P1.3 in a pull up state (As is the case in LunchBox), and we need to read the value of the pin.

Here is a snippet of code example for testing individual bits in a register:



```
if ((P1IN & BIT3) == 0)
    //to be done when P1.3 = 0
else
    // to be done when P1.3 = 1
```
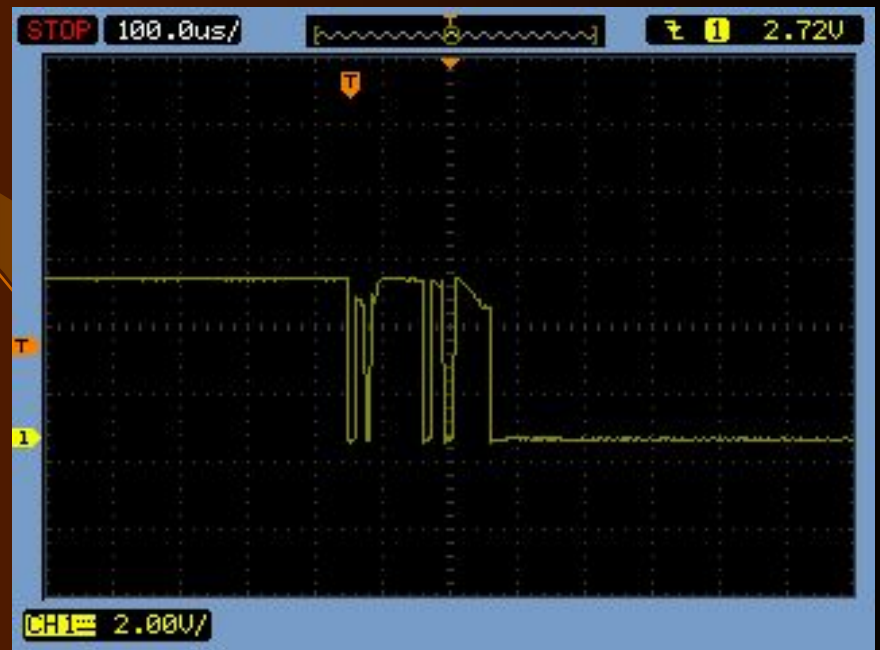
# Switch Bouncing

- Common problem associated with the mechanical switches and relays.
- Made up of spring metals which are forced to contact each other by an actuator.
- While they collide each other there is a possibility of rebounding for some time before they make a stable contact.



# Hardware Debouncing

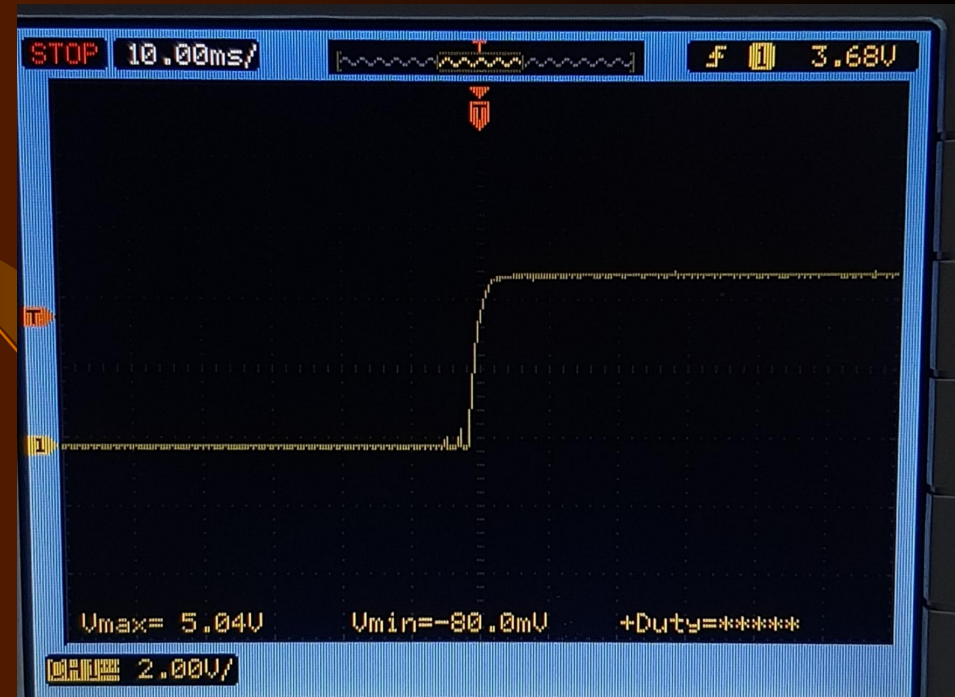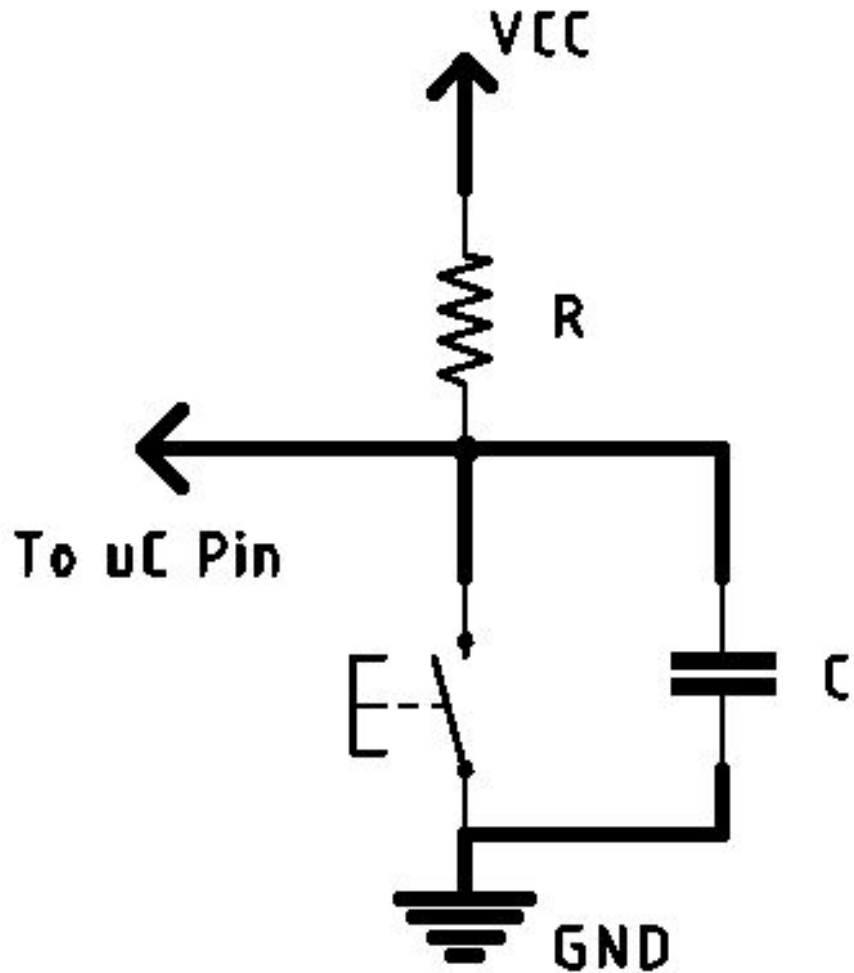

# Software Debouncing

- Provide a delay of  $\sim 20$  milliseconds after the first change is detected.





Let's start programming!