

Introduction to Embedded System Design

Physical Interfacing- 2

Dhananjay V. Gadre

Associate Professor

ECE Division

Netaji Subhas University of
Technology, New Delhi


Badri Subudhi

Assistant Professor


Electrical Engineering Department

Indian Institute of Technology,
Jammu

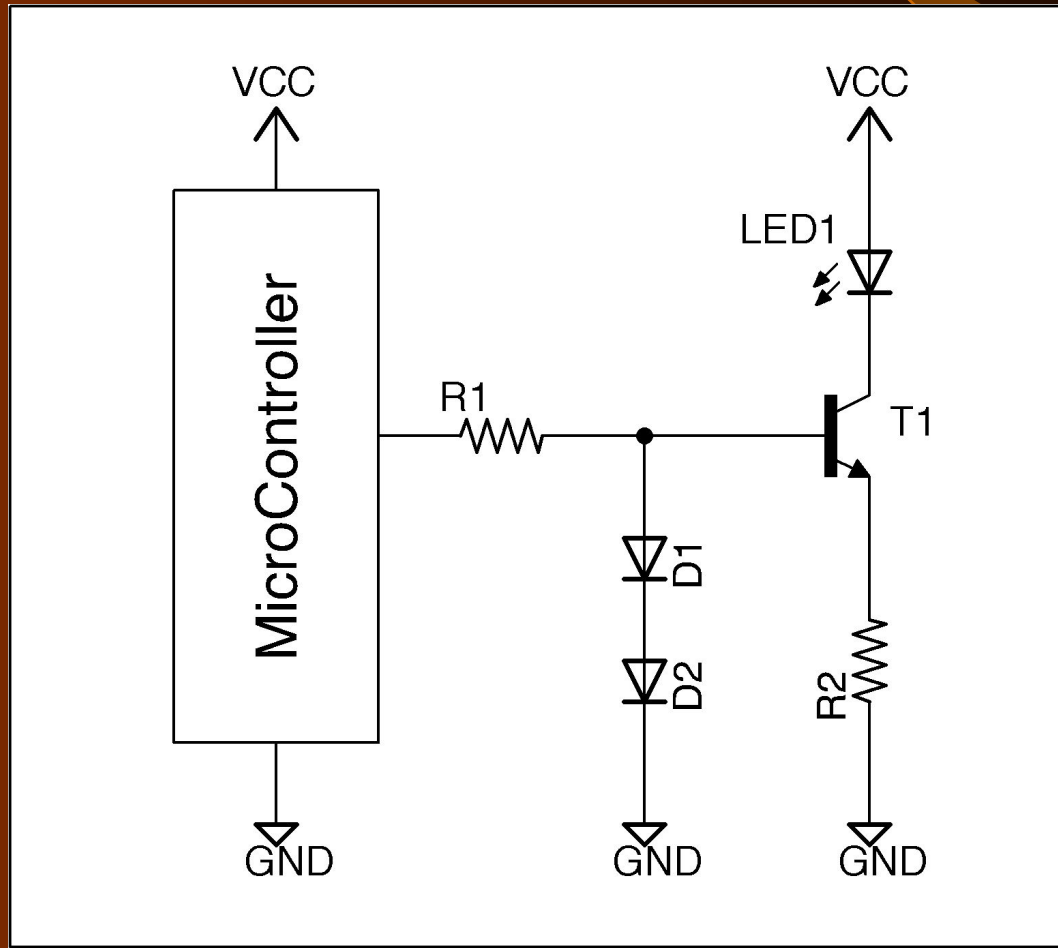
Driving LEDs (Or Other loads): Constant Current Low Side Driver



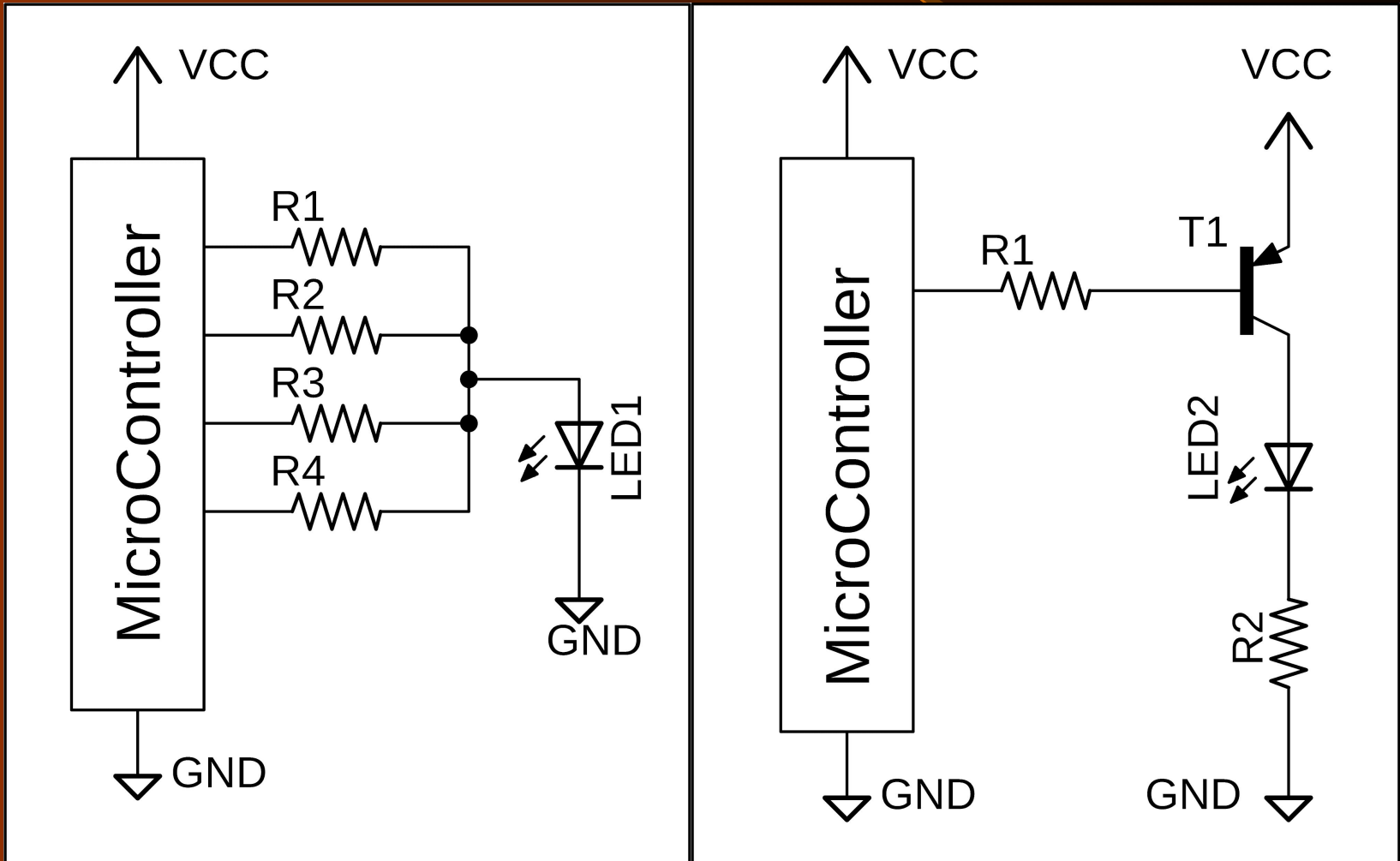
Driving LEDs (Or Other loads): High Side Driver



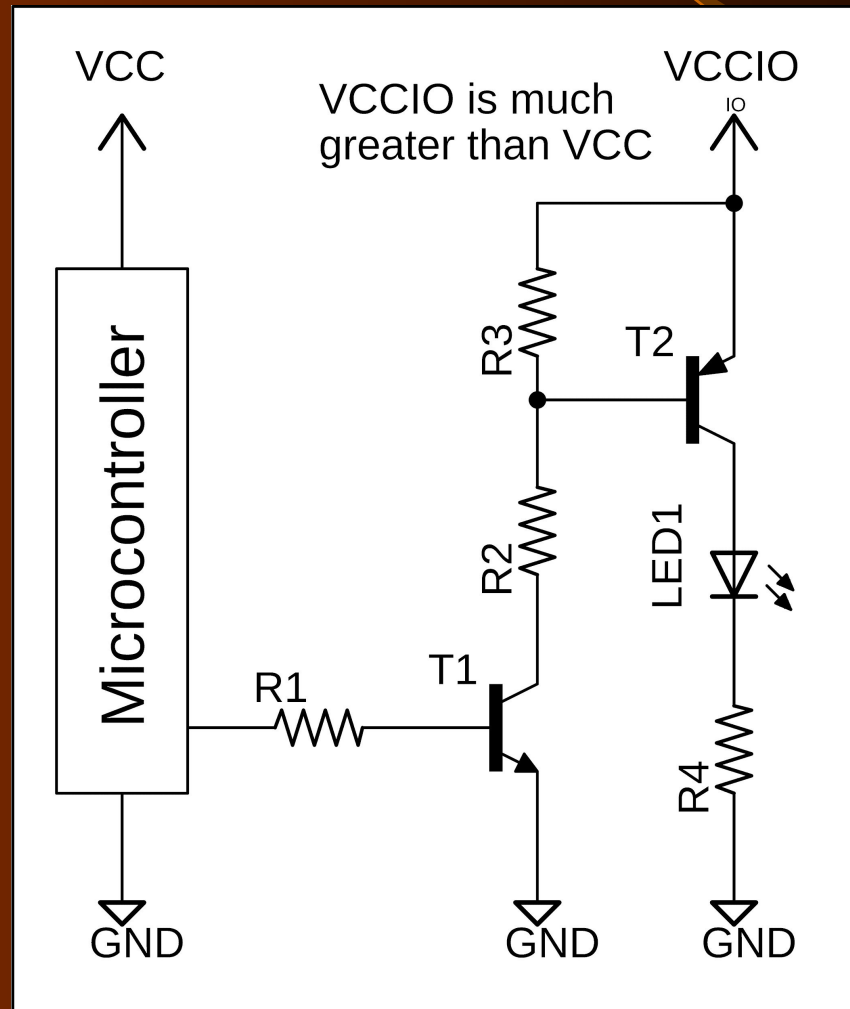Driving LEDs (Or Other loads): High Side Driver



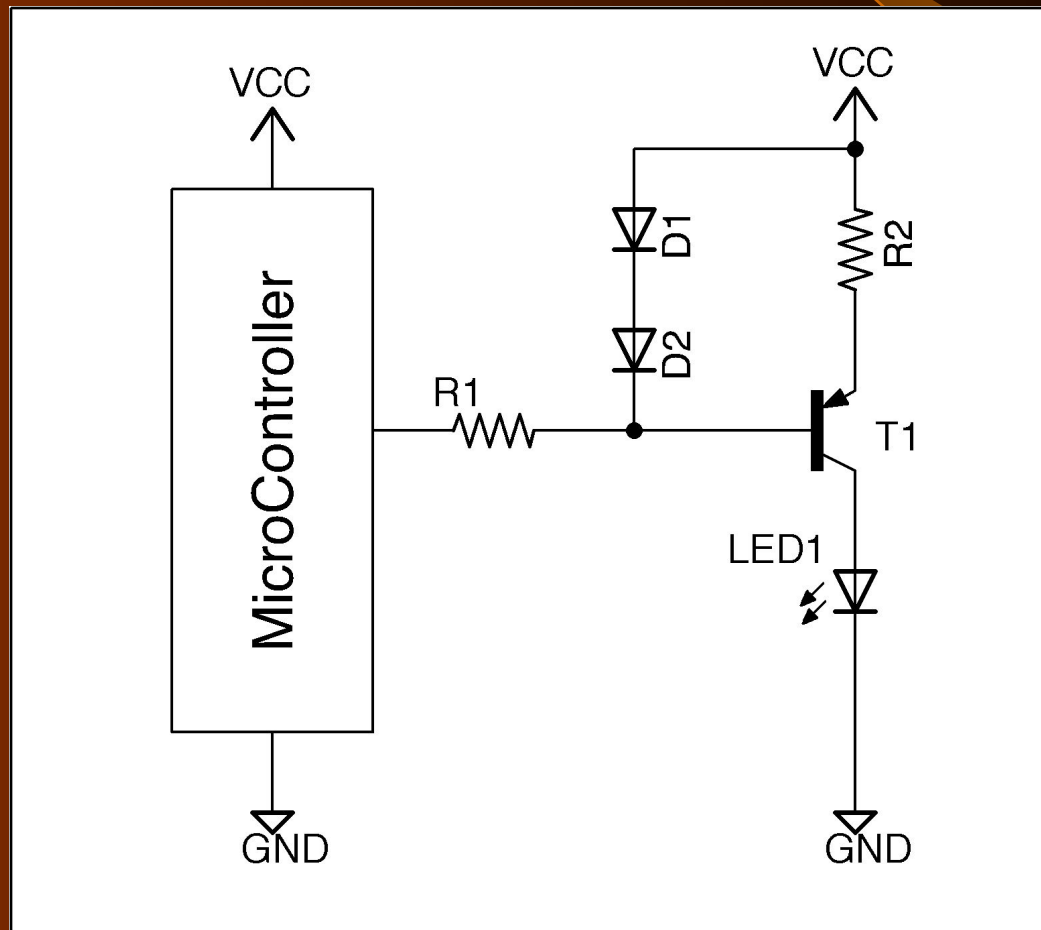
Driving LEDs (Or Other loads): Constant Current High Side Driver





Controlling LEDs

- N pins \rightarrow N LEDs?
- N pins $\rightarrow (N^2)/4$ LEDs?
(Multiplexing)
- N pins $\rightarrow N*(N-1)$ LEDs?
(Charlieplexing)


Driving Seven Segment Displays

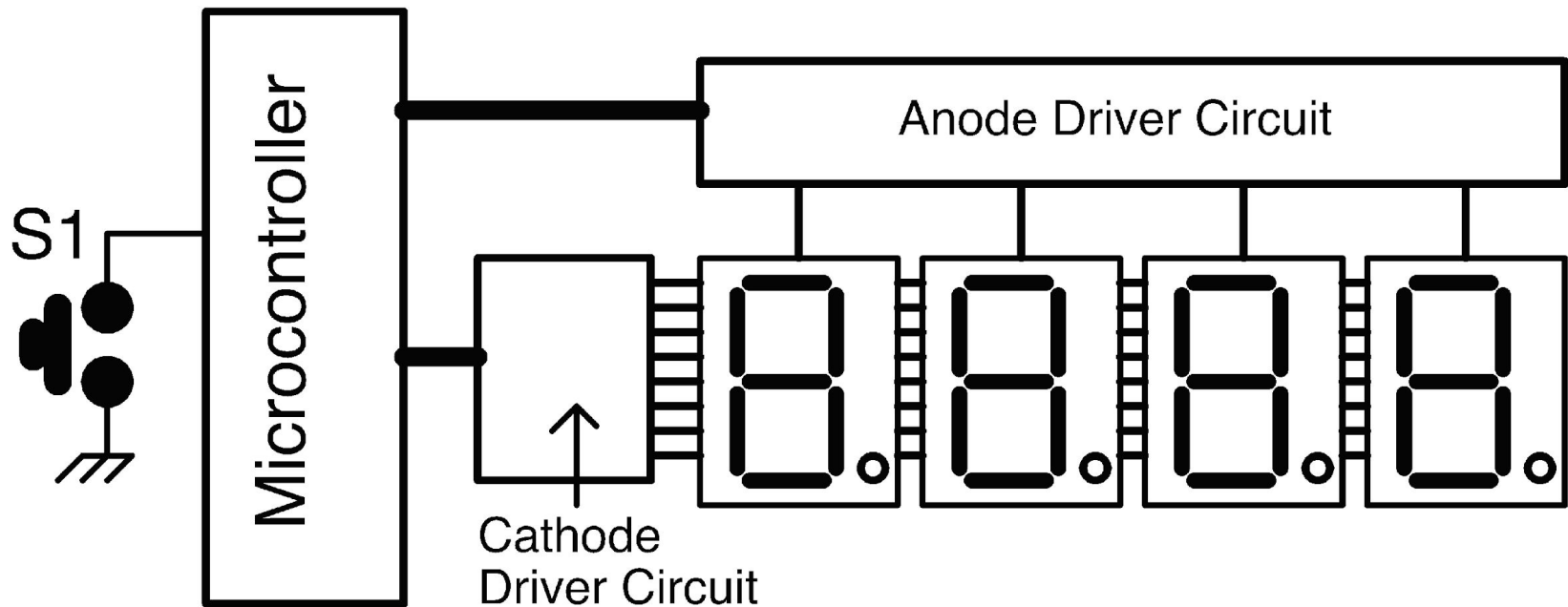


Low Side Driver

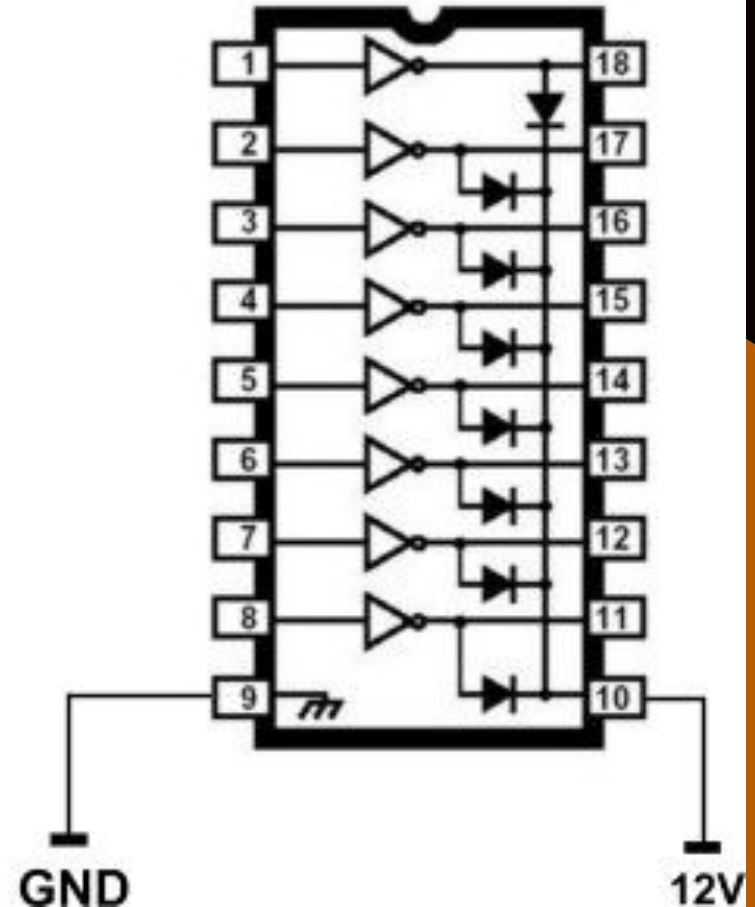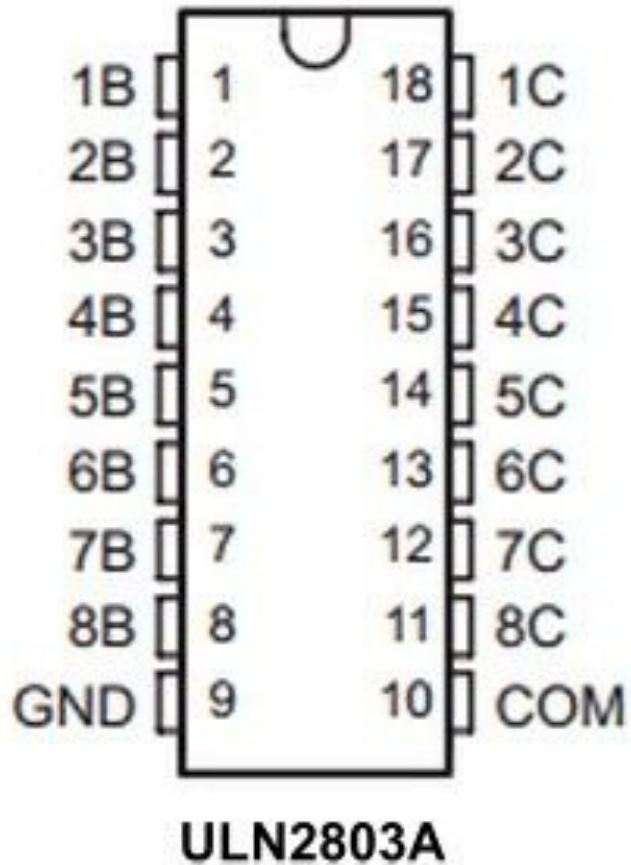


High Side Driver

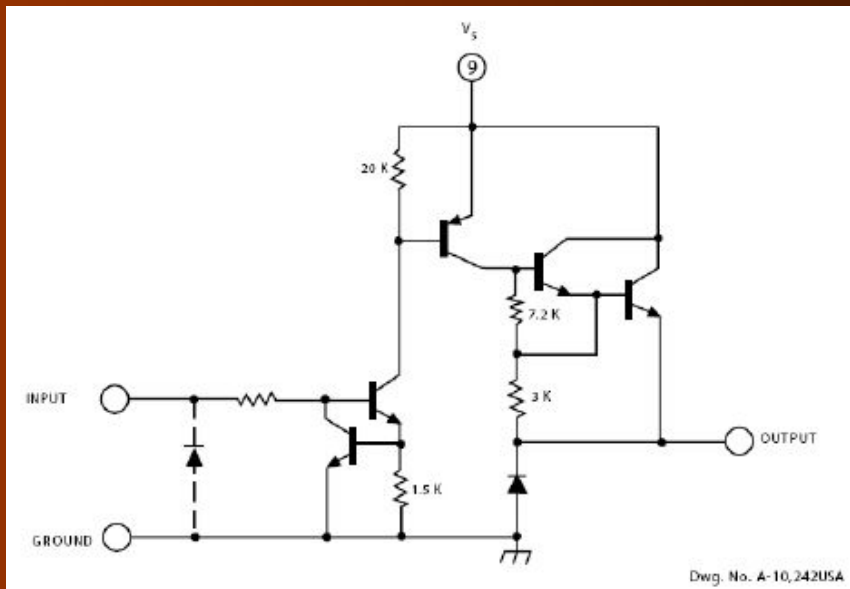


UDN2981A thru UDN2984A

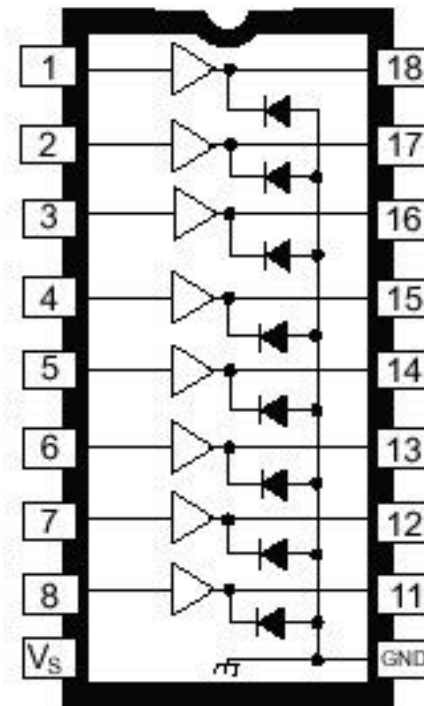

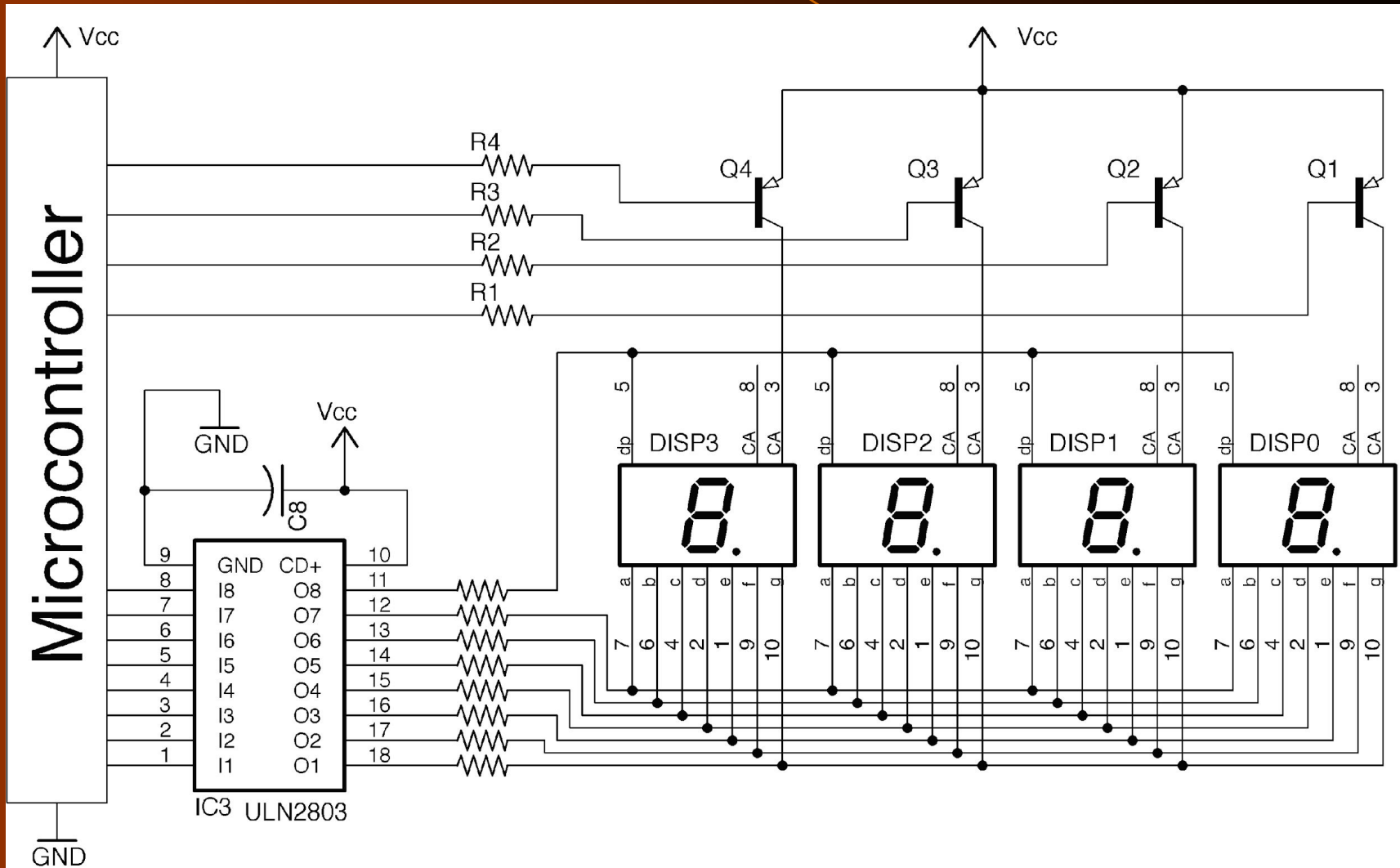
Both Side Switching: Driving Seven Segment Displays



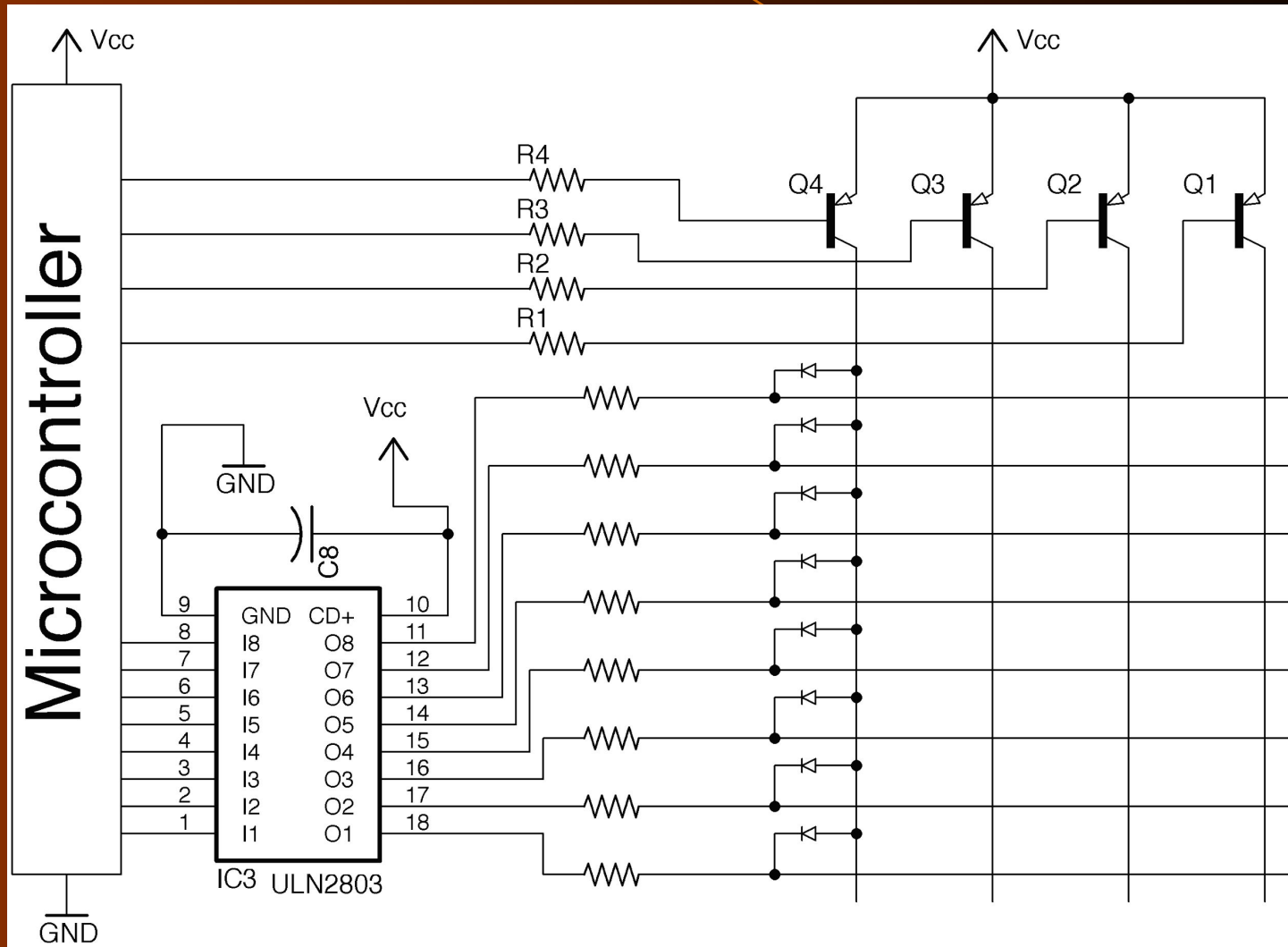Both Side Switching: Driving Dot Matrix Displays




Alternate Method of Both Side Switching

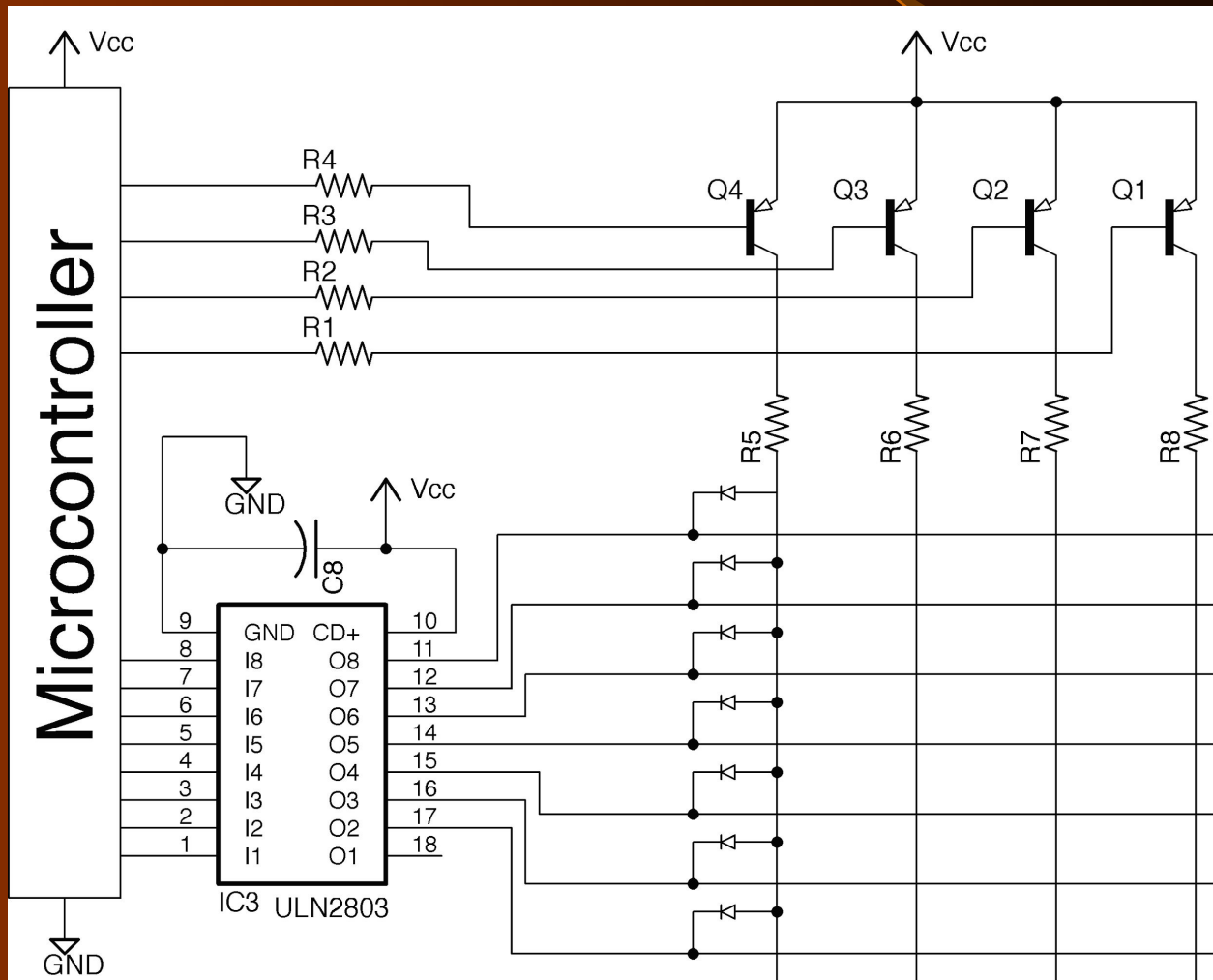


Charlieplexing


N pins \rightarrow $N*(N-1)$ LEDs

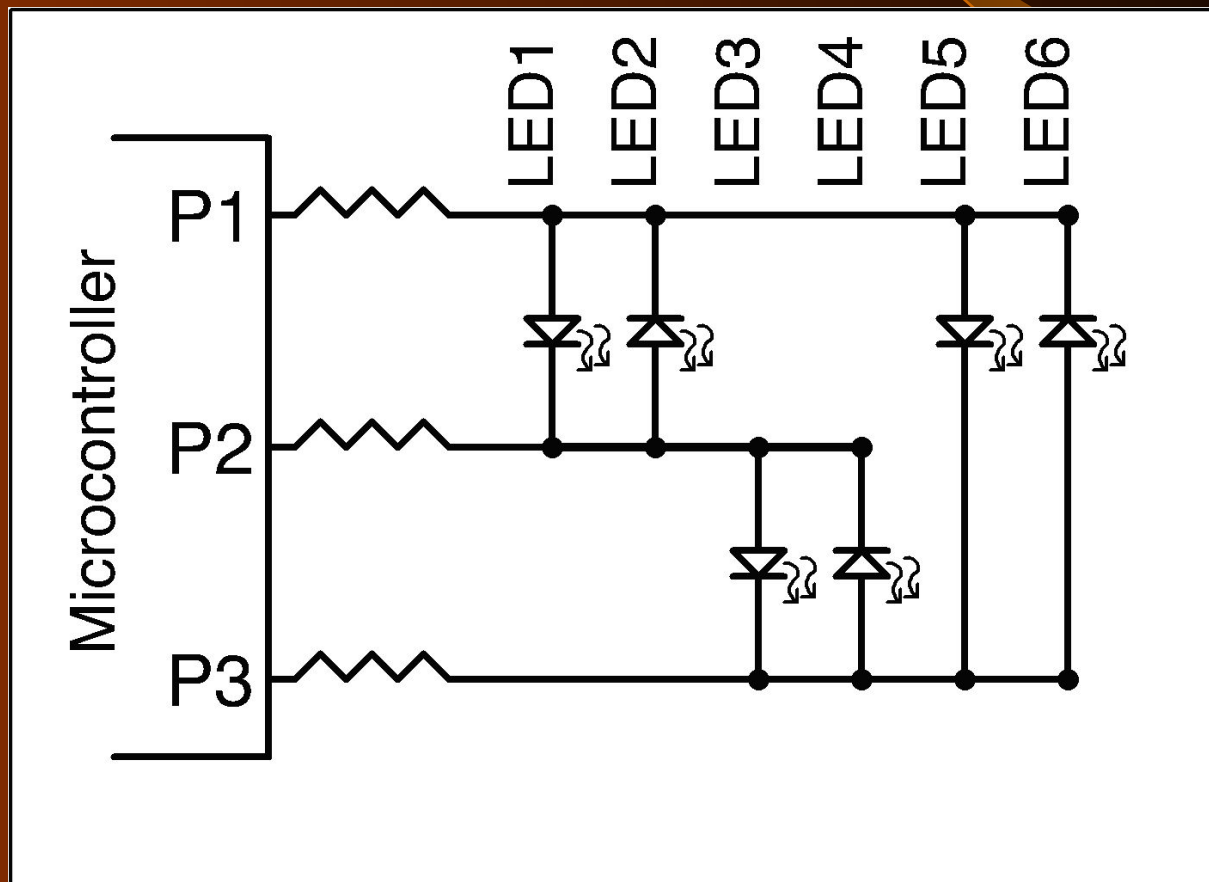


Digital to Analog Conversion: Using PWM

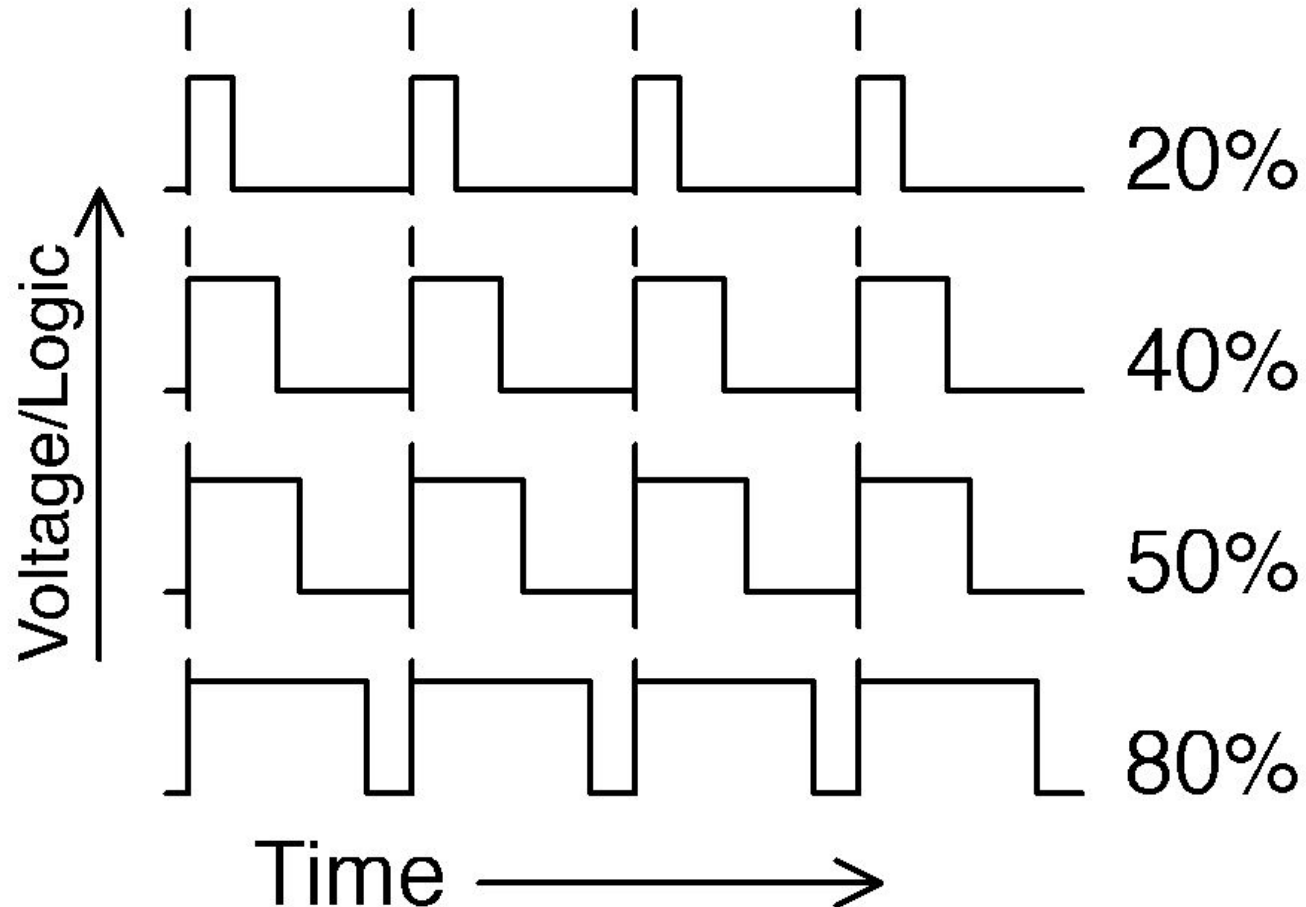

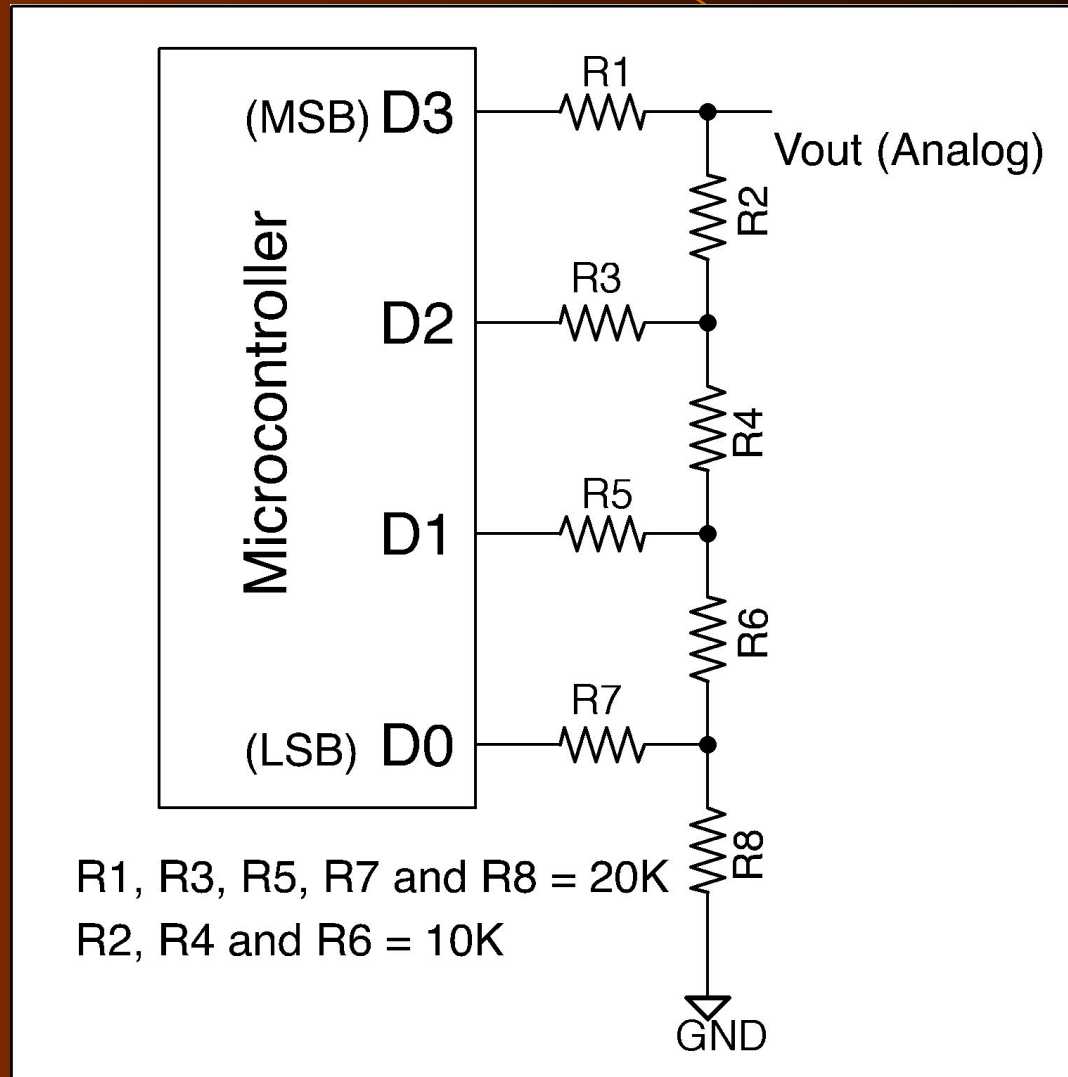Digital to Analog Conversion: Using R-2R Ladder DAC



Liquid Crystal Displays

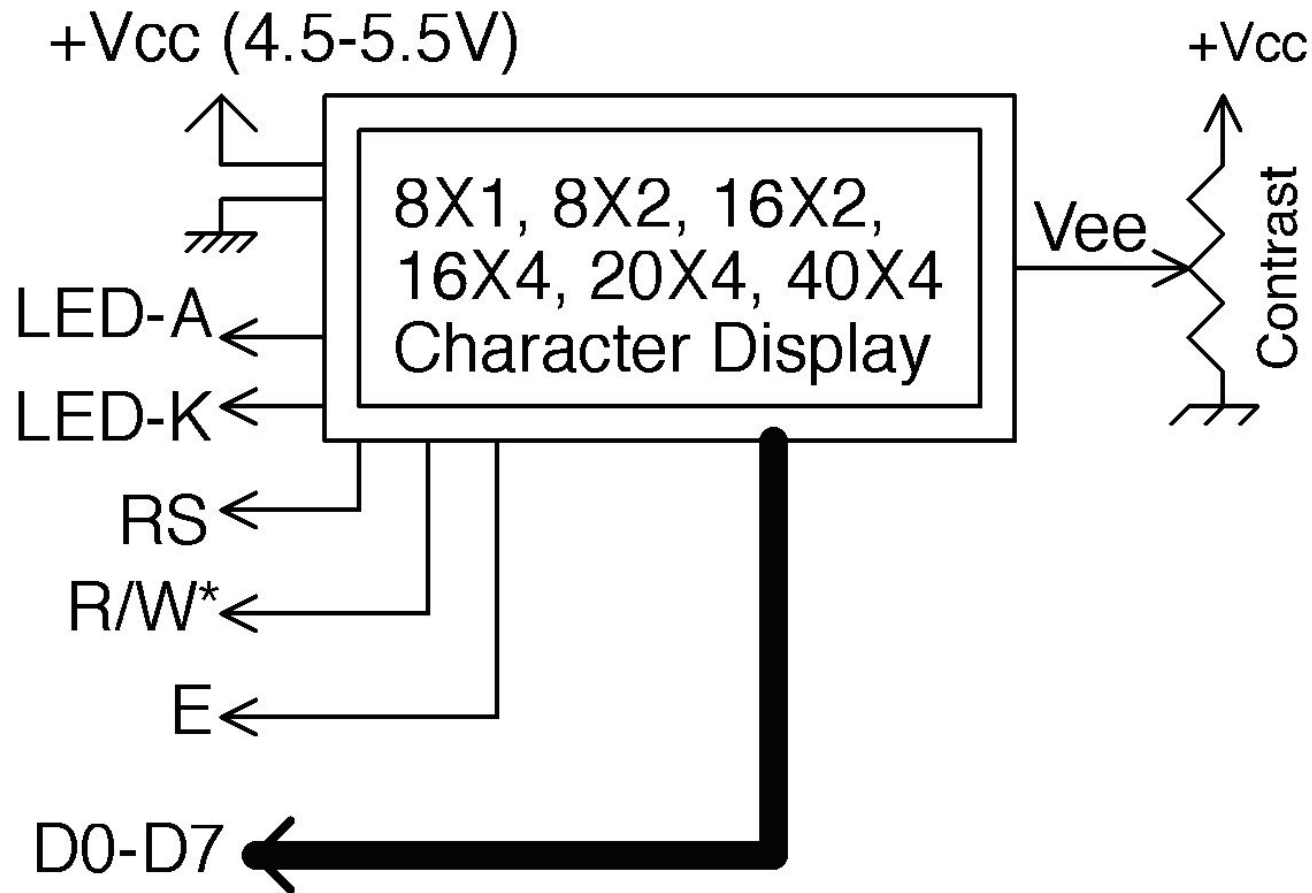

Hitachi HD LCD Controller (5x8 dot-matrix)

Liquid Crystal Displays

+Vcc (2.7-3.3V)

LED+

CS*

RST

D/C

Din

Sclk



Nokia
Graphics
Display
(48x84 pixels)

Buzzer and Speaker

- **Buzzer: In-built driver**
- **External driver: Tuned circuit actuated using timer.**
- **Speaker: Transistor switch and Timer**
- **DAC + Audio amplifier**

Ultrasonic

- **Piezoelectric element with a strong resonance**

Haptic

- **DC Motor with eccentric load**



Thank you!